

# Digital Systems

Digital HW design with VHDL in a nutshell

R. Pacalet

Telecom Paris

2024-02-22



## 1 Introduction

# Section 1

## Introduction

# Digital hardware: 2 types of hardware primitives

## Combinatorial gates

- inverters, and, or, xor, 1-bit full adders, 1-bit multiplexers
- inputs  $\Rightarrow$  boolean computation  $\Rightarrow$  outputs
- inputs change  $\Rightarrow$  electrical signals propagate
- propagation delay
  - performance
  - critical path
  - maximum clock frequency
- no loops


# Digital hardware: 2 types of hardware primitives

## Memory elements

- latches, D-flip-flops, RAMs...
- data inputs, control inputs and data outputs
- do not react immediately to any inputs changes
- react on a particular combination of control inputs
- example: rising-edge triggered D-flip-flop (DFF)
  - clock input
  - data input
  - clock rising edge  $\Rightarrow$  data input sampled
  - data output = currently sampled input
  - data output stable until next rising edge of clock
  - even if the data input changes in between
- think of a digital camera
  - clock = press button
  - data input = scene
  - data output = displayed picture


# Example of a sequential circuit

Reusing the same hardware

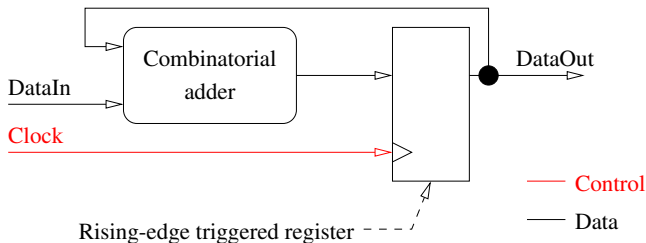

# Example of a sequential circuit


## Pipelined circuit

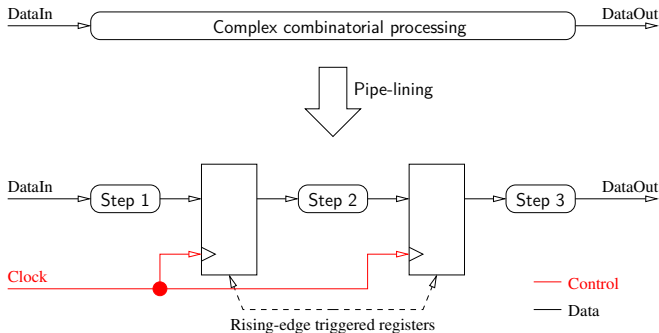
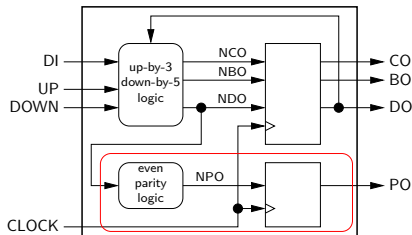
# Synchronous process

Output signals are register outputs

```
process(clock)
begin
  if rising_edge(clock) then
    o <= f(i);
  end if;
end process;
```





Output signals cannot be combinatorial outputs

```
process(clock)
begin
    if rising_edge(clock) then
        o <= f(i);
    end if;
end process;
```

